
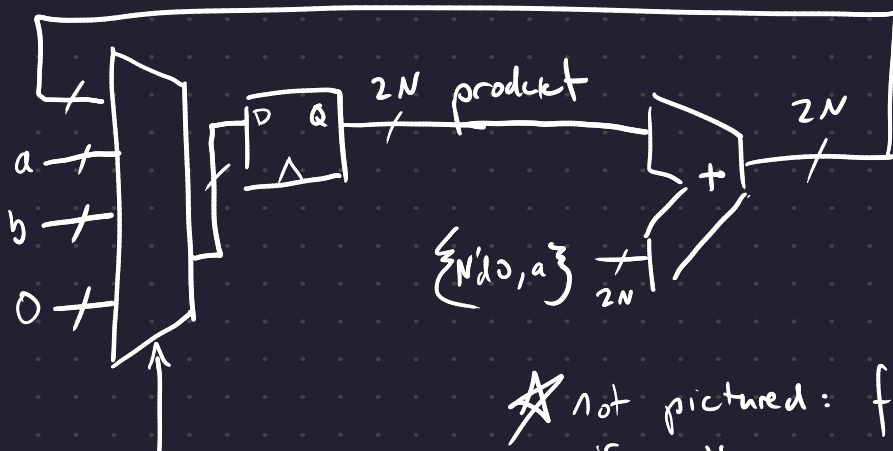
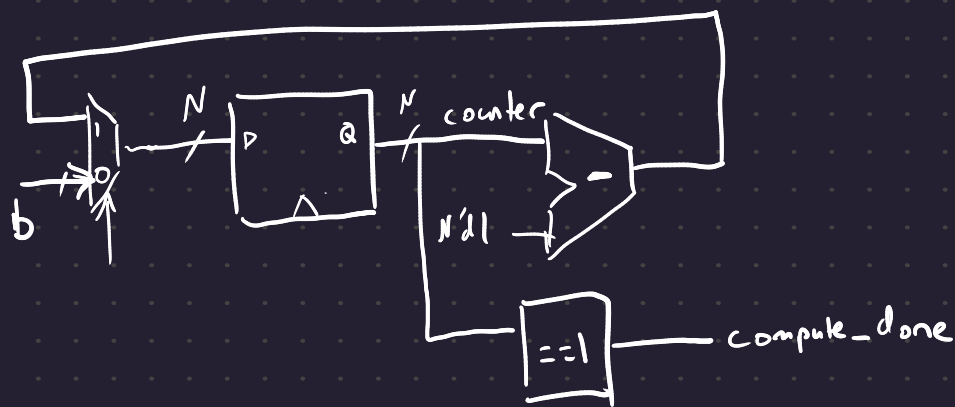


MULTIPLIER FSM

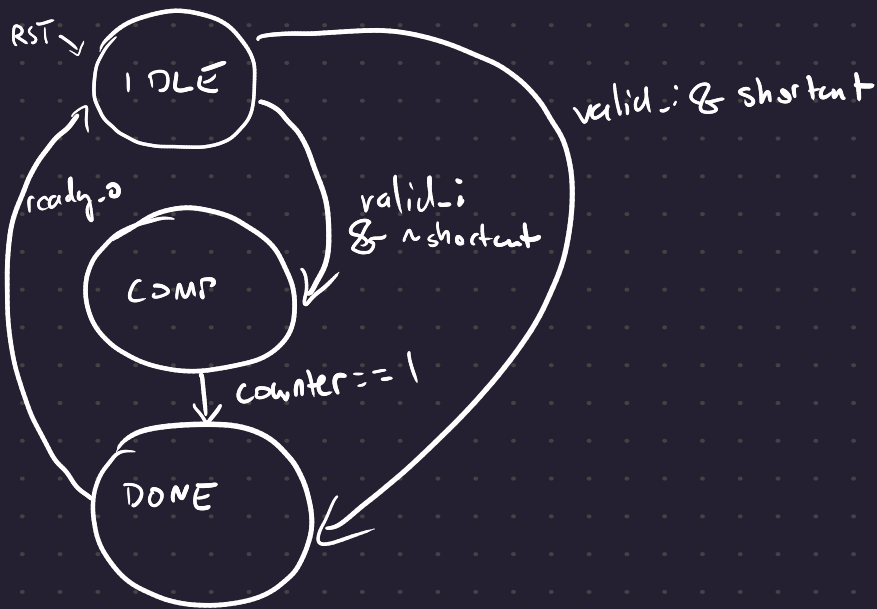

See shortcut logic.

★ not pictured: flops are only enabled if the FSM requires it.

Approach: add a to itself b times.

At start of compute, initializing a COUNTER to b , and an ACCUMULATOR to a .

Each cycle, increment the ACCUMULATOR by a , and decrement COUNTER.

After B cycles, assert that the result is valid!

Wait till Main asserts ready_0 to go back to IDLE.

Optimization of Special Cases

if $a == 0$, or $b == 0$, result is zero.

if $a == 1$, result is b and vice versa.

clever muxing can save states!